

# INDRAPRASTHA INSTITUTE of INFORMATION TECHNOLOGY DELHI

# Department of Electronics & Communication Engineering

Embedded Logic Design(ECE270)

Dr. Sumit J Darak

Lab\_4: Design and implement an overlapping sequence detector using

Mealy FSM and verify its functionality

**Mohammad Shariq** 

2020220 16-10-2021

#### **OBJECTIVE:**


- ➤ 1. Design and implement an overlapping sequence detector using Mealy FSMand verify its functionality using testbench.
- ➤ 2. Design a clock pulse generator.
- ➤ 3. Test the functionality of the design on the Basys 3 Board (remote access) using VIO IP.

Topics to Explore:1) Mealy and Moore FSM implementation, 2) Use of 3 Always blocks, 3) Difference between overlapping and non-overlapping


#### **Theory:**
 
## • Clock pulse Generator

The first thing we need to consider is the **clock pulse generation** for the FSM. We will use a 200 Hz clock to generate a clock pulse, which transitions from 0 to 1 whenever any of the data push buttons is pressed. The following block diagram will give you an abstract view of the implementation(all the ports are not shown).



#### • *FSM*:

 

# **Observations:**

# programme for functionality of FSM

```
KUJECT MANAGER - FSM
  Project Summary × fsm_11011.v
  D:/IIITD/ELD\_LABs/LAB\_4\_Moorey\_and\_Melley\_FSM/FSM.srcs/sources\_1/new/fsm\_11011.v
  Q 🗎 🛧 🥕 🐰 🖺 🛍 🗙 // 🖩 🗘
      `timescale 1ns / 1ps
   3 | // Company:
     // Engineer:
   5 //
   6 / // Create Date: 13.10.2021 11:38:12
      // Design Name:
      // Module Name: fsm 11011
  9
      // Project Name:
  10 // Target Devices:
  11 // Tool Versions:
  12
     // Description:
  13
  14 // Dependencies:
  15 | //
  16 // Revision:
  17
      // Revision 0.01 - File Created
  18 / // Additional Comments:
  19 //
  21
  22
  23 module fsm 11011(
  24
  25
         input clear,
  26
         input inp_1,
  27
        input input_pulse,
  28
        output reg out=0,
  29
         output reg [2:0] present_state
  30
  31
  32
        reg[2:0] next_state;
       narameter 80=3'h000 81=3'h0001 82=3'h010 83=3'h011 84=3'h100 //narameter are defined so that we don't need to remember the
  33 :
```

#### **PROJECT MANAGER** - FSM Sources Project Summary × fsm\_11011.v D://IIITD/ELD\_LABs/LAB\_4\_Moorey\_and\_Melley\_FSM/FSM/FSM.srcs/sources\_1/new/fsm\_11011.v Q 🔛 🔸 🥕 🐰 🖺 🖿 🗙 🖊 🖩 🗘 Source File Properties 31 32 reg[2:0] next state; 33 parameter S0=3'b000,S1=3'b0001,S2=3'b010,S3=3'b011,S4=3'b100; //parameter are defined so that we don't need to remember the 34 // also it makes the code more readable 35 36 37 🖯 always @(posedge input\_pulse or posedge clear) 38 ⊝ begin 39 🖨 if(clear ==1'b1) 40 present\_state<=S0; 41 42 🖨 present\_state<=next\_state; 43 44 🖯 45 46 🖯 always @(\*) 47 ⊝ begin 48 next\_state = present\_state; 49 🖯 case (present\_state) 50 ⊖ S0:if (inp\_1==1'b1) 51 next\_state =S1; 52 else 53 🖨 next state=S0; 54 🖯 S1:if (inp 1==1'b1) 55 next\_state =S2; 56 else 57 🖨 next\_state=S0; 58 🖨 S2:if (inp\_1==1'b0) 59 next\_state =S3; 60 else 61 🖨 next state=S2; 62 63 🗀 83.if (inn 1==1!h1)

24

84 \(\hat{\text{-}}\) endmodule

85

72

D:/IIITD/ELD\_LABs/LAB\_4\_Moorey\_and\_Melley\_FSM/FSM/FSM.srcs/sources\_1/new/fsm\_


Source File Properties

```
54 🖨
                     S1:if (inp_1==1'b1)
55
                             next state =S2;
56
                        else
57 🖯
                              next_state=S0;
58 ⊖
                     S2:if (inp_1==1'b0)
59
                             next state =S3;
60
                        else
61 🗇
                              next state=S2;
62
63 <del>(</del>
                     s3:if (inp 1==1'b1)
64
                             next_state =S4;
65
                        else
66 🖯
                              next_state=S0;
67 □
                     S4:if (inp 1==1'b1)
68
                             next state =S2;
69
                        else
70 🖨
                              next state=S0;
71
72 |
                     default : next state=S0;
73 🖯
               endcase
74 🖯
            end
75 |
76 ⊖
       always @(posedge input pulse)
77 🖯
        begin
78 ⊖
                 if (present_state==S4 && inp_1 == 1'b1)
79
                         out<=1;
80
                 else
81 🖨
                     out<=0;
82 🗇
        end
83
```

# Testbench for FSM

```
fsm_tb.v
D:/IIITD/ELD_LABs/LAB_4_Moorey_and_Melley_FSM/FSM.srcs/sim_1/new/fsm_tb.v
Q 🔡 ← → 🐰 🖺 🛍 🗙 // 🖩 🗘
16 // Revision:
17 | // Revision 0.01 - File Created
18 // Additional Comments:
19 //
21
22
23 module fsm_tb(
24
25
       );
26
27
       reg clear,input_pulse , inp_1;
28
       wire [2:0] present_state;
29
       wire out;
30 |
31
       fsm_11011 tb1(.input_pulse(input_pulse),.clear(clear),.inp_1(inp_1),.out(out),.present_state(present_state));
32
33 🗦
       initial begin
34
          input_pulse<=1'b0;
35
           clear<=1'b1;
36
          inp_1<=1'b0;
37
38 ⊝
39 ¦
40 🖨
       initial begin
41
42
       #5 clear=0;
43
       @(posedge input_pulse) inp_1<=1; // changing the input data at negative edge of the clock*
44
       @(posedge input_pulse) inp_1<=1;
45 :
       @(posedge input_pulse) inp_1<=0;
46
       @(posedge input_pulse) inp_1<=1;
       @(posedge input_pulse) inp_1<=1; // pattern is completed
47
48
       @(posedge input_pulse) inp_1<=0;
49
       @(posedge input_pulse) inp_1<=1;
50 ¦
       @(posedge input pulse) inp 1<=1; // overlaped pattern is completed again
51
52 🖨
53 ¦
    always #10 input_pulse=~input_pulse;
55
56 ← endmodule
57 :
```

# Results for automated testbench:

 

# • program for functionality Pulse\_Generaor:


```
Project Summary
             × fsm_11011.v × pulse_tb.v × input_pulse.v
D:/IIITD/ELD_LABs/LAB_4_Moorey_and_Melley_FSM/FSM/FSM.srcs/sources_1/new/input_pulse.v
                 X 🖹 🖿 X //
   // Additional Comments:
   : //
19
21
22
23 module input pulse(
24
        input clk 200H,
        input inp_0, //7: ;iv, idput as 7
25
        input inp_1, //7: plye .1Apst as 1
26
       output input pulse
27
28
   );
29
30
      req Q= 0;
      reg D = 0;
31
32
33
        wire inp pulse;
34
35
        assign inp_pulse= inp_0 | inp_1;
36
37 □
       always @(posedge clk_200H)
38 ⊖
       begin
39
           Q <= D;
40 🖯
        end
41
42 🖯
      always @(*) begin
43
           D= inp_pulse;
44 🖯
        end
45
        assign input pulse=Q;
46
47 dendmodule
48
49
```

# • Testbench program for functionality Pulse\_Generaor:


■ Default Layor

```
Project Summary × fsm_11011.v × pulse_tb.v × input_pulse.v
D:/IIITD/ELD_LABs/LAB_4_Moorey_and_Melley_FSM/FSM/FSM.srcs/sim_1/new/pulse_tb.v
   21
22
23 module pulse tb(
24
25 i
      );
26
27
     reg clk, inp_0,inp_1;
28
    wire input_pulse;
29
30
      input_pulse tb0(.clk_200H(clk),.inp_0(lnp_0) ,.inp_1(inp_1) , .input_pulse(input_pulse));
31
32 ⊖
      initial
33 🖯
        begin
34 i
             clk = 0;
35 ¦
             inp 0 = 0; inp 1 = 0;
36 🖒
          end
37
38 🖵
      initial begin
39
         #5 inp_0=0; inp_1 =1;
         #7 inp 0=0; inp 1=0;
40 i
41
42 🖯
        // for doing another test
43 i
         //# inp 0=0; inp 1=1;
44 🖯
          // #inp 0=0; inp 1=0;
45 🖨
      end
46
47
      always #10 clk = -clk;
48
49 🖨 endmodule
50
```


### Test Result for Input Pulse:

 


 
# Constraints for the implementation and VIO module programme



## VIO Wrapper Settings:

 

 


 


```
d:/IIITD/ELD\_LABs/LAB\_4\_Moorey\_and\_Melley\_FSM/FSM/FSM.srcs/sources\_1/ip/vio\_0/vio\_0.veo
   // Applications"). Customer assumes the sole risk and
   // liability of any use of Xilinx products in Critical
   // Applications, subject only to applicable laws and
42
   // regulations governing limitations on product liability.
43
   //
44
    // THIS COPYRIGHT NOTICE AND DISCLAIMER MUST BE RETAINED AS
   // PART OF THIS FILE AT ALL TIMES.
4.5
46
47
    // DO NOT MODIFY THIS FILE.
48
    // IP VLNV: xilinx.com:ip:vio:3.0
49
50
    // IP Revision: 20
51
52
   // The following must be inserted into your Verilog file for this
53
    // core to be instantiated. Change the instance name and port connections
54
    // (in parentheses) to your own signal names.
55
56
     //----- Begin Cut here for INSTANTIATION Template ---// INST TAG
    vio_0 your_instance_name (
57
58
     .clk(clk),
59
     .probe_in0(probe_in0),
                              // input wire [2 : 0] probe in1
     .probe_in1(probe_in1),
60
     .probe_out0 (probe_out0), // output wire [0 : 0] probe_out0
61
62
     .probe_out1(probe_out1),
63
      .probe_out2 (probe_out2) // output wire [0 : 0] probe_out2
64
65
   // INST_TAG_END ----- End INSTANTIATION Template -----
66
67
    // You must compile the wrapper file vio 0.v when simulating
68
    // the core, vio 0. When compiling the wrapper file, be sure to
    // reference the Verilog simulation library.
69
```


```
Q 🛗 ← → 🐰 🖺 🛍 🗙 // 🖩 🗘
   // Description:
13
   // Dependencies:
14
15 //
16 // Revision:
17
    // Revision 0.01 - File Created
18 // Additional Comments:
19 ! //
21
22
23 🖯 module vio_wrapper4(
24
      input clk
25
26
2.7
       wire clear, inp_0,inp_1,out;
28
      wire[2:0] present_state;
29
30
       vio_0 vio4(
31
    .clk(clk),
                            // input wire clk
    .probe_in0(out), // input wire [0 : 0] probe_in0
32
     .probe_in1(present_state), // input wire [2 : 0] probe_in1
.probe_out0(inp_0), // output wire [0 : 0] probe_out0
33
34
     .probe_out1(inp_1), // output wire [0 : 0] probe_out1
35
     .probe_out2(clear) // output wire [0 : 0] probe out2
36
37
38
39
40
        topSeq tb5(.clk_100M(clk),.clear(clear),.input_0(inp_0),.input_1(inp_1),.out(out),.present_state(present_state));
41
42 ndmodule
43
```

#### BitStream Generated Successfully:

 

 
 
#### Testing on BASYS3 Board using VIO IP



#### **Conclusion:**

Successfully tested functionality of an overlapping Sequence detector using Mealy FSM on BASYS3 board using VIO IP (Remote Access).